

During the interval  $\Delta$  when both the switches are off, the inductor current splits equally between the two secondary half-windings and  $v_{oi} = 0$ . Therefore,  $t_{on} < t < t_{on} + \Delta$ ,

$$v_L = -V_o$$

and

$$i_{D1} = i_{D2} = \frac{1}{2}i_L$$

The next half-cycle consists of  $t_{on}$  (during which  $T_2$  is on) and the interval  $\Delta$ . The waveforms repeat with a period  $\frac{1}{2}T_s$  and

$$t_{on} + \Delta = \frac{1}{2}T_s$$

Equating the time interval of the inductor voltage during one repetition period  $\frac{1}{2}T_s$  using Eqs. 10-22, 10-23, and 10-25 yields

$$\frac{V_o}{V_d} = 2 \frac{N_2}{N_1} D \quad 0 < D < 0.5$$

where  $D = t_{on}/T_s$  is the duty ratio of switches 1 and 2 and the maximum value it can have is 0.5 (in practice, to maintain a small blanking time to avoid turning both the switches on simultaneously,  $D$  should be kept smaller than 0.5). The average value of the inductor current waveform in Fig. 10-13b equals  $V_o$ .

It should be noted that in the push-pull inverter of Chapter 8, the feedback diodes connected in antiparallel to the switches were required to carry the reactive current. In their conduction interval depended inversely on the power factor of the output load. In a push-pull dc-dc converter, these antiparallel diodes shown dotted in Fig. 10-13a are needed to provide a path for the current required due to leakage flux of the transformer.

In push-pull circuits, due to a slight and unavoidable difference in the switching times of two switches  $T_1$  and  $T_2$ , there is always an imbalance between the peak values of the two switch currents. This imbalance can be eliminated by means of current-mode control of the converter, which is discussed later in this chapter.

#### 10-4-5 HALF-BRIDGE CONVERTER (DERIVED FROM STEP-DOWN CONVERTER)

Figure 10-14a shows a half-bridge dc-dc converter. As discussed in Chapter 8 in connection with the half-bridge inverters, the capacitors  $C_1$  and  $C_2$  establish a voltage midpoint between zero and the input dc voltage. The switches  $T_1$  and  $T_2$  are turned on alternatively, each for an interval  $t_{on}$ . With  $T_1$  on,  $v_{oi} = (N_2/N_1)(V_d/2)$  as shown in Fig. 10-14b and, therefore,

$$v_L = \frac{N_2}{N_1} \frac{V_d}{2} - V_o \quad 0 < t < t_{on}$$

During the interval  $\Delta$ , when both switches are off, the inductor current splits equally between the two secondary halves. Assuming ideal diodes,  $v_{oi} = 0$ , and therefore,

$$v_L = -V_o \quad t_{on} < t < t_{on} + \Delta$$

In steady state, the waveforms repeat with a period  $\frac{1}{2}T_s$  and

$$t_{on} + \Delta = \frac{1}{2}T_s$$



Figure 10-14 Half-bridge converter.

Equating the time interval of the inductor voltage during one repetition period  $\frac{1}{2}T_s$  using Eqs. 10-27 through 10-29 yields

where  $D = t_{on}/T_s$  and  $V_d = V_d/2$ . The diodes in an antiparallel connection as in a push-pull converter.

#### 10-4-6 FULL-BRIDGE STEP-DOWN CONVERTER

Figure 10-15a shows a full-bridge converter with two pairs of switches  $T_1, T_2$  and  $T_3, T_4$  turned on alternatively. The output voltage  $v_{oi} = (N_2/N_1)V_d$ , and